

Write the following information in the first page of Answer Script before starting answer

**ODD SEMESTER EXAMINATION: 2020-21**

Exam ID Number \_\_\_\_\_

Course \_\_\_\_\_ Semester \_\_\_\_\_

Paper Code \_\_\_\_\_ Paper Title \_\_\_\_\_

Type of Exam: \_\_\_\_\_ (Regular/Back/Improvement)

**Important Instruction for students:**

1. Student should write objective and descriptive answer on plain white paper.
2. Give page number in each page starting from 1<sup>st</sup> page.
3. After completion of examination, Scan all pages, convert into a single PDF, rename the file with Class Roll No. (2019MBA15) and upload to the Google classroom as attachment.
4. Exam timing from 10am – 1pm (for morning shift).
5. Question Paper will be uploaded before 10 mins from the schedule time.
6. Additional 20 mins time will be given for scanning and uploading the single PDF file.
7. Student will be marked as ABSENT if failed to upload the PDF answer script due to any reason.



10. When  $A', B'$  are the inputs to a NAND gate, according to De- Morgan's theorem, the output expression could be
- $X = A+B$
  - $X = (AB)'$
  - $X = (A)(B)$
  - None of the above
11. How many AND gates are required to realize  $Y = CD + EF + G$ ?
- 4
  - 5
  - 3
  - 2
12. The number of min-terms after minimizing the following Boolean expression is \_\_\_\_\_.
- $[D' + AB' + A'C + AC'D + A'CD]'$
- 1
  - 2
  - 3
  - 4
13. A decoder converts N inputs to \_\_\_\_\_ outputs
- N
  - $N^2$
  - $2^N$
  - $N^N$
14. How many truth table entries are necessary for a four-input circuit?
- 4
  - 8
  - 12
  - 16
15. A full adder can be made out of \_\_\_\_\_
- Two half adders
  - Two half adders and OR gate
  - Two half adders and NOT gate
  - Three half adders
16. Which device has one input and many outputs ?
- De multiplexer
  - Multiplexer
  - Counter
  - Flip-flop
17. In a sequential circuit, the output at any time depends only on the input values at that time.
- Past output values
  - Intermediate values
  - Both past output and present input
  - Present input values
18. A ripple counter is a (n):
- Asynchronous Counter
  - Synchronous Counter
  - Parallel Counter
  - None of the above
19. The D flip-flop has \_\_\_\_\_ inputs
- 1
  - 3
  - 2
  - 4
20. The function  $AB'C + A'BC + ABC' + A'B'C + AB'C'$  is equivalent to
- $A'B + AC' + AC$
  - $A'B' + A'C' + AC$
  - $AB' + AC' + A'C$
  - None of the above

**(PART-B : Descriptive)**

Time: 2 hrs. 40min.

Marks:50

**[ Answer question no. 1 & any four (4) from the rest ]**

1. Write truth table and logic diagram for five very important gates in digital system. 10
2. Minimize the following with the help of K-map and draw the logic circuit for the minimized expression. 5+5=10
  - a.  $F = \Sigma(2,3,4,5,6,7,9,12,13,14,15)$
  - b.  $F = ac' + a'b'c' + a'b + ab$
3. How many types of shift registers are available? Explain each of them with diagram. 10
4. a. How we create a Master- Slave flip flop using two JK flip flop? 4+6=10  
b. Explain mod-14 negative edge asynchronous up counter with diagram.
5. a. Write the truth table and draw logic circuit diagram for full adder which consist of two half adders and one OR gate. 5+5=10  
b. Explain octal to binary encoder.
6. a. Perform the following subtractions using 1's and 2's complement methods: 4+4+2=10
  - i.  $1101_{(2)} - 1010_{(2)}$
  - ii.  $10101_{(2)} - 10111_{(2)}$  
b. Convert  $4AB_{16}$  to binary.
7. Simplify the following expression 4+6=10
  - a.  $X = [AB'(C+BD) + A'B']C$
  - b.  $X = A' + AB + AC' + AB'C'$
8. Write short notes on any two: 5+5=10
  - a. SR Flip Flop with NAND gate
  - b. Synchronous Down counter
  - c. 16:1 Multiplexer

= = \*\*\* = =