

BACHELOR OF COMPUTER APPLICATION
Second Semester
DIGITAL LOGIC & DESIGN
(BCA - 06)

Duration: 3Hrs.

Full Marks: 70

PART A (Objective) =20
PART-B (Descriptive)=50

PART-B (Descriptive)

Duration: 2 hrs. 40 mins.

Marks: 50

1. Answer the following questions (any five):

2×5=10

- a) Covert $(378.98)_{10}$ to Octal.
- b) Obtain 1's and 2's compliment of the following:
 - iii) 1010101
 - iv) 0111000
- c) State and prove Distributive and Idempotence laws of Boolean algebra.
- d) Construct the truth table for AND and OR gate.
- e) Explain DeMorgans law.
- f) What do you mean by Don't Care Condition?
- g) What is Sequential Circuit Explain?

2. Answer the following questions (any five):

3×5=15

- a) What do you mean by shift registers? Explain.
- b) Briefly explain binary ripple counter.
- c) Write a short note on ASCII and EBCDIC codes.
- d) What do you mean by Number System? Write about any 2 number systems.

- e) Explain logic gates for XOR, NAND and NOR gates with the help of logic circuit diagram.
- f) Explain J-K flip flop with its logic diagram.
- g) What are Registers and Counters, explain.

3. Answer the following questions (any five):

5×5=25

- a) Describe the operations performed by the Half-adder and Full-adder arithmetic circuit.
- b) Explain the working principle of Decimal Adder.
- c) Obtain the truth table for:
$$F = xy + xy' + y'z$$
$$F = xy + x'y' + y'z$$
- d) Simplify the following function using K-map:
$$F = A'B'CD' + A'B'CD + AB'CD' + AB'CD + A'BCD + A'BC'D$$
- e) Briefly explain decoders with the help of a diagram.
- f) Explain design of a simple computer with block diagram.
- g) Briefly explain clocked R-S flip flop with the help of logic diagram.

BACHELOR OF COMPUTER APPLICATION
Second Semester
DIGITAL LOGIC & DESIGN
(BCA - 06)

Duration: 20 minutes

Marks – 20

PART-A (Objective)

Time: 20 mins

Total Marks: 20

I. Choose the correct option:

1×20=20

- How many states do a binary variable has?
a) 2 b) 3 c) 4
- The NAND function is complement of which function:
a) OR b) XOR c) AND
- A computer system is sometimes divided into 2 functional entities, they are:
a) Hardware & Software
b) OS & Software
c) CPU & OS
- A function of 'n' variables will have how many minterms:
a) 2^n b) $2n$ c) 2
- A combinational circuit that performs the arithmetic addition of 2 bits is called:
a) Half adder b) Full adder c) JK Flip Flop
- The input variables of a half adder is called:
a) Augend & addend b) Sum & carry c) Bits
- Base of decimal number system is:
a) 2 b) 8 c) 10
- Binary equivalent of $(C6)_{16}$ is:
a) 11000110 b) 11110000 c) 00010011
- An illustration that is used to visualise the relationships among the variables of a Boolean expression is:
a) Venn Diagram b) Logic circuit c) K-map
- Symbol ' Σ ' stands for:
a) ORing of terms b) ANDing of terms c) XORing of terms

- Each square in K-map represents:
a) One minterm b) One maxterm c) One variable
- A four variable K-map will have:
a) 2 minterms b) 16 minterms c) 8 minterms
- A decoder converts binary information from 'n' input lines into how many unique output lines:
a) 2 b) 2^n c) 2^2
- A flip flop has 2 useful states:
a) Input & output b) Set & clear c) A & B
- A flip flop sensitive to pulse duration is called:
a) Latch b) Register c) Master Slave
- A register capable of shifting its binary information either to left or right is called:
a) Shift register b) Register c) Flip flop
- $x(y+z) = xy + xz$ is an example of:
a) Demorgans law b) Involution law c) Distributive law
- $(x+y)' = x'y'$ is an example of:
a) Commutative law b) Demorgans law c) Absorption law
- The 'inverter logic gate' has:
a) 1 input, 1 output b) 2 inputs, 1 output c) 2 input, 2 outputs
- MSI counters come in 2 categories:
a) Ripple counters, synchronous counters
b) Half adder, full adder
c) JK flip flop, RS flip flop
