

**B.SC. ELECTRONICS
SEMESTER- 3RD
ANALOG ELECTROICS
BSE-302**

Duration: 3 Hrs.

Marks: 70

PART : A (OBJECTIVE) = 20
PART : B (DESCRIPTIVE) = 50

[PART-B : Descriptive]

Duration: 2 Hrs. 40 Mins.

Marks: 50

[Answer question no. One (1) & any four (4) from the rest]

1. Discuss the effect of middle frequency in RC coupled amplifier. 10

2. (a) What are the different types of open loop OP-AMP configuration? (6+4=10)
Discuss with the help of diagram.

(b) State Barkhausen criterion of oscillation.

3. (a) Explain with the help of diagram the construction of Multistage transistor amplifier. (6+4=10)

(b) Write short notes on CMRR.

4. (a) In a negative feedback amplifier, $A=100$, $\beta=0.04$ and $V_s=50$ mV . Find (4+6=10)

(i) gain without feedback (ii) output voltage
(iii) feedback factor (iv) feedback voltage.

(b) Derive the expression for change in input impedance in voltage-series-feedback.

5. (a) Show that the percentage change in gain with feedback is much less than percentage change in gain without feedback. (6+4=10)
(b) Explain the concept of virtual ground.

6. (a) Explain the working of the oscillatory circuit with the help of necessary diagram. (6+4=10)
(b) Find the expression for overall efficiency in Class B power amplifier.

7. (a) Explain the construction and operation of RC phase-shift oscillator. (8+2=10)
(b) Draw the transfer characteristics of OP-AMP.
8. (a) Explain with the help of diagram the construction of Hartley oscillator. (5+5=
(b) Show that the output is equal to the average of the three three inputs in Summing amplifier.

==***==

**B.SC. ELECTRONICS
SEMESTER-3RD
ANALOG ELECTROICS
BSE-302**

[PART-A : Objective]

Choose the correct answer from the following :

1X20=20

1. In voltage –series feedback, input resistance
 - a. Increases
 - b. Decreases
 - c. Does not change
 - d. None of the above
2. When the collector current flows at all times during full cycle of signal, the operation is known as
 - a. Class A operation
 - b. Class B operation
 - c. Class C operation
 - d. None of the above
3. For the negative feedback,
 - a. $A_f=A$
 - b. $A_f<A$
 - c. $A_f>A$
 - d. All of the above
4. In case of positive feedback,
 - a. $A_f=0$
 - b. $A_f=1$
 - c. $A_f=\infty$
 - d. All of the above
5. The range of audio frequency oscillator is
 - a. 20 Hz-20 kHz
 - b. 20 kHz-30 MHz
 - c. 30 MHz-300 MHz
 - d. None of the above
6. The Barkhausen criterion of oscillation is
 - a. $A\beta=0$
 - b. $A\beta=1$
 - c. $A\beta=2$
 - d. Both (a) and (b)
7. In RC Phase Shift Oscillator, the phase angle in each RC section is
 - a. 90 degree
 - b. 180 degree
 - c. 60 degree
 - d. 360 degree
8. The overall efficiency in class B amplifier is
 - a. 50%
 - b. 30%
 - c. 75.5%
 - d. 78.5%
9. The open-loop voltage gain of an ideal OP-AMP is
 - a. Zero
 - b. Infinite
 - c. 1
 - d. 10
10. In inverting OP-AMP, the output is given by
 - a. $+AV_{id}$
 - b. $-AV_{id}$
 - c. A/V_{id}
 - d. All of the above
11. The potential difference between two terminals in virtual ground is
 - a. Infinite
 - b. Zero
 - c. 1
 - d. All of the above
12. In middle frequency range, coupling capacitor in RC-Coupled amplifier is
 - a. Very large
 - b. Small
 - c. Neglected
 - d. None of the Above
13. The reciprocal of sensitivity is called
 - a. Stabilization of gain
 - b. Desensitivity
 - c. Distortion
 - d. None of the above
14. In Hartley Oscillator , the tank circuit consists of
 - a. One inductor and two variable capacitors
 - b. One variable capacitor and two inductors
 - c. One inductor and one variable capacitor
 - d. One inductor, one capacitor and one resistance

15. The total phase shift in Hartley Oscillator is
- 180 degree
 - 360 degree
 - 120 degree
 - None of the above
16. In a sub -tractor, the output voltage is equal to
- The difference of two input voltages
 - Sum of two input voltages
 - Zero
 - Unity
17. A multi stage amplifier consists of
- Input stage and output stage
 - Intermediate stage
 - Level shifting stage
 - All of the above
18. An Oscillator is a device that
- Generates an alternating voltage
 - Generates an ac output without requiring the input
 - Converts d.c. energy into a.c. energy at very high frequency
 - All of the above
19. The Colpitt's oscillator consists of
- Two inductor & two capacitor
 - Two capacitor & one inductor
 - Two inductor and one capacitor
 - All of the above
20. Regarding the negative feedback in amplifier which statement is wrong?
- It widens the separation between 3-db frequencies
 - It increases the gain bandwidth product
 - It improves the gain stability
 - It reduces distortion

==***==

UNIVERSITY OF SCIENCE & TECHNOLOGY, MEGHALAYA



[PART (A) : OBJECTIVE]

Duration : 20 Minutes

Serial no. of the
main Answer sheet

Course :

Semester : Roll No :

Enrollment No : Course code :

Course Title :

Session : 2017-18 Date :

Instructions / Guidelines

- The paper contains twenty (20) / ten (10) questions.
- Students shall tick (✓) the correct answer.
- No marks shall be given for overwrite / erasing.
- Students have to submit the Objective Part (Part-A) to the invigilator just after completion of the allotted time from the starting of examination.

Full Marks	Marks Obtained
20	

.....
Scrutinizer's Signature

.....
Examiner's Signature

.....
Invigilator's Signature