

B.Sc. PHYSICS
THIRD SEMESTER
DIGITAL SYSTEMS & APPLICATIONS
BSP – 303 OLD COURSE [REPEAT]
[USE OMR FOR OBJECTIVE PART]

**SET
A**

Duration: 3 hrs.

Full Marks: 70

Time: 30 min.

(Objective)

Marks: 20

Choose the correct answer from the following:

1X20=20

- The binary addition $1+1+1$ gives
 - 111
 - 10
 - 110
 - 11
- The number 1000_2 is equivalent to decimal number
 - One thousand
 - Eight
 - Four
 - Sixteen
- The only function of a NOT gate is to
 - Stop a signal
 - Re-complement a signal
 - Invert an input signal
 - Act as a universal gate
- A NOR gate is ON only when all its inputs are
 - ON
 - Positive
 - High
 - OFF
- An S-R latch is a
 - Combinational circuit
 - Synchronous circuit
 - One bit memory element
 - One clock delay element
- In a sequential circuit the output state depends upon
 - Past output states and present input states
 - Input states only
 - Input and output states
 - None of these
- According to the algebra of logic, $(A + \bar{A})$ equals
 - A
 - 1
 - 0
 - $\bar{A}\bar{A}$
- The expression \overline{ABC} can be simplified to
 - $\bar{A} \cdot \bar{B} \cdot \bar{C}$
 - $\bar{A}B + \bar{B}C + \bar{C}A$
 - $\bar{A}B + \bar{C}$
 - $\bar{A} + \bar{B} + \bar{C}$
- D-Flip flop can be configured from a
 - J-K Flip flop and a \bar{A} inverter
 - R-S Flip flop
 - R-S Flip flop and an inverter
 - J-K Flip flop

10. Boolean algebra is essentially based on
- | | |
|------------|------------|
| a. Symbols | b. Logic |
| c. Truths | d. Numbers |
11. The frequency of oscillation of an astable multi-vibrator depends mainly on the
- | | |
|-------------------------------------|-----------------------------|
| a. Value of collector load resistor | b. RC value of the circuit |
| c. Value of transistor β | d. Width of the input pulse |
12. First integrated circuit chip was developed by
- | | |
|---------------|------------------|
| a. C.V. Raman | b. W.H. Brattain |
| c. J.S. Kilby | d. Robert Noyce |
13. An integrated circuit is
- | | |
|---|--------------------------------------|
| a. A complicated circuit | b. An integrated device |
| c. Much costlier than a single transistor | d. Fabricated on a tiny silicon chip |
14. Most important advantage of an IC is its
- | | |
|--|-------------------------------|
| a. Easy replacement in case of circuit failure | b. Extremely high reliability |
| c. Reduced cost | d. Low power consumption |
15. A microprocessor is ALU
- | | |
|--|--|
| a. And control unit on a single chip | b. And memory on a single chip |
| c. Register unit and I/O device on a single chip | d. Register unit and control unit on a single chip |
16. The signal to be viewed on the screen of an oscilloscope is applied
- | | |
|--------------------------------|-----------------------------|
| a. Across its X-Plate | b. Across its Y-Plate |
| c. To the horizontal amplifier | d. To the triggered circuit |
17. The digital system usually operates on _____ system.
- | | |
|-----------|----------------|
| a. Binary | b. Decimal |
| c. Octal | d. Hexadecimal |
18. A logic gate is an electronic circuit which
- | | |
|----------------------------|---|
| a. Makes logic decision | b. Allows electron flow only in one direction |
| c. Works on binary algebra | d. Alternates between 0 and 1 values |
19. According to the Absorptive Laws of Boolean algebra, expression $(A + AB)$ equals
- | | |
|-------|----------------|
| a. A | b. B |
| c. AB | d. $A \cdot A$ |
20. The time period of IC-555 mono-stable multivibrator operation is
- | | |
|------------|------------|
| a. 1.38 RC | b. 1.1 RC |
| c. 1.45 RC | d. 13.8 RC |

(Descriptive)

Time: 2 hrs. 30 min.

Marks: 50

[Answer question no.1 & any four (4) from the rest]

1. What is the advantage of J-K Flip flop over S-R Flip flop? How is an S-R Flip flop converted to J-K Flip flop? Write the truth table for J-K flip flop and convert it to characteristics table and excitation table. 2+4+4
=10

2. a. What is a binary coded decimal? Write the following numbers in BCD code : 157, 2498 and 673. 4+3+3
=10
b. Write the steps involved in 2's complement subtraction. Use 2's complement to subtract 1010_2 from 1101_2 .
c. Find the decimal equivalent of the following binary numbers: 101_2 , 1001_2 and 10.011_2 .

3. a. Draw the equivalent diode relay circuit of an AND gate and explain the operation. 4+4+2
=10
b. Sketch the symbol and construct the truth table for XOR and NAND gates.
c. Draw a logic circuit for the Boolean expression
$$y = \bar{A} \cdot B \cdot C + (A + B) \cdot \bar{C}$$

4. a. Using the truth table, prove that $A + AB = A + B$ and illustrate the equivalence with the help of a switching circuit. 4+2+4
=10
b. Simplify the Boolean expression
$$ABC + A\bar{B}\bar{C} + \bar{A}BC + ABC + A\bar{B}C$$

c. Prove the Boolean identity $(A+B)(A+C) = A+BC$

5. a. Draw the block diagram, write the truth table for a hexadecimal to binary Encoder and implement it using logic gate. 6+4=10
b. Construct a 8×1 MUX using a 4×1 MUX.
6. a. With the help of a neat and labeled diagram explain the working of an astable multi-vibrator. 8+2 =10
b. The components of IC-555 Timer astable multi-vibrator is given as: $R_A=7.5\text{ k}\Omega$, $R_B= 7.5\text{ k}\Omega$, $C= 0.1\mu\text{F}$, $V_{CC}= 5\text{ V}$. Determine the frequency.
7. a. Mention the advantages of ICs. 5+5=10
b. Differentiate between Linear ICs and Digital ICs.
8. Draw the block diagram of the 8085A Microprocessor. Explain its organization and operation. 5+5=10

== *** ==